

Parallel generation of ℓ -sequences

Cédric Lauradoux

Université de Princeton

Andrea Röck

Équipe SECRET, INRIA

Journées "Codage et Cryptographie" 2008

Outline

- ▶ Introduction

- ▶ LFSRs
 - Synthesis of sub-sequences
 - Multiple steps LFSR


- ▶ FCSRs
 - Synthesis of sub-sequences
 - Multiple steps FCSR

- ▶ Conclusion

Part 1

Introduction

Sub-sequences generator

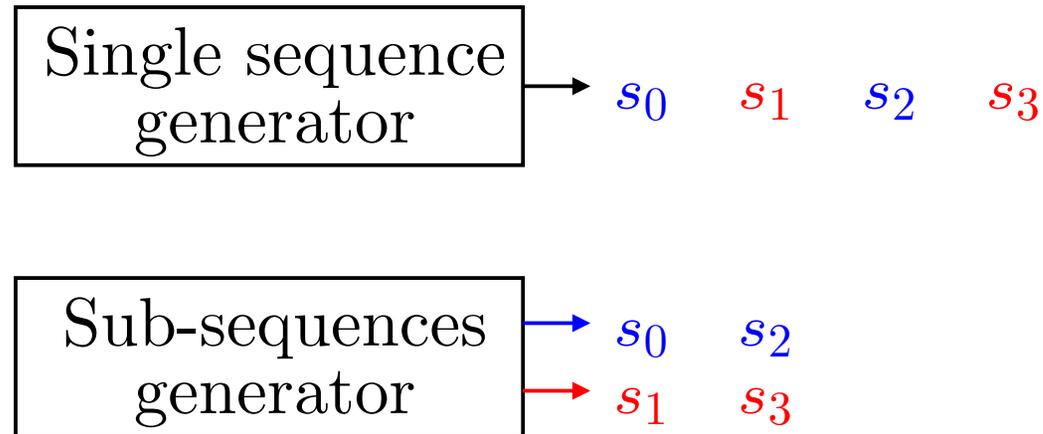

► Goal: **parallelism**

- better throughput
- reduced power consumption

Notations

- ▶ $S = (s_0, s_1, s_2, \dots)$: Binary sequence with period T .
- ▶ $S_d^i = (s_i, s_{i+d}, s_{i+2d}, \dots)$: Decimated sequence, with $0 \leq i \leq d - 1$.
 - $S_d^0 = (s_0, s_d, \dots), \dots, S_d^{d-1} = (s_{d-1}, s_{2d-1}, \dots)$
- ▶ x_j : Memory cell.
- ▶ $(x_j)_t$: Content of the cell x_j .
- ▶ X_t : Entire internal state of the automaton.
- ▶ $next^d(x_j)$: Cell connected to the output of x_j .

LFSRs


- ▶ Automaton with linear update function.
- ▶ Let $s(x) = \sum_{i=0}^{\infty} s_i x^i$ be the power series of $S = (s_0, s_1, s_2, \dots)$. There exists two polynomials $p(x), q(x)$:

$$s(x) = \frac{p(x)}{q(x)}.$$


- ▶ $q(x)$: Connection polynomial of degree m .
- ▶ $Q(x) = x^m q(1/x)$: Characteristic polynomial.
- ▶ m -sequence: S has maximal period of $2^m - 1$.
(iff $q(x)$ is a primitive polynomial)
- ▶ Linear complexity: Size of smallest LFSR which generates S .

Fibonacci/Galois LFSRs

Fibonacci setup.

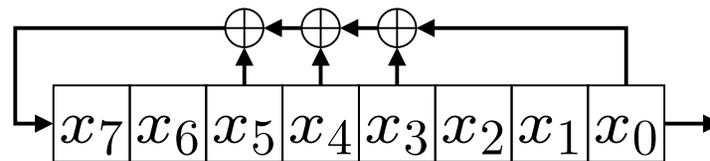

Galois setup.

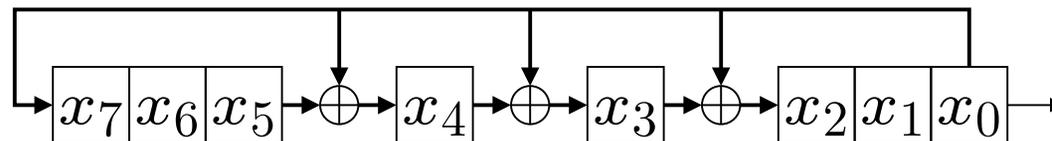

FCSRs


[Klapper Goresky 93]

- ▶ Instead of XOR, FCSRs use **additions with carry**.
 - **Non-linear** update function.
 - **Additional memory** to store the carry.
- ▶ S is the **2-adic expansion** of the rational number: $\frac{h}{q} \leq 0$.
- ▶ **Connection integer q** : Determines the feedback positions.
- ▶ **ℓ -sequences**: S has maximal period $\varphi(q)$.
(*iff* q is a prime power and $\text{ord}_q(2) = \varphi(q)$.)
- ▶ **2-adic complexity**: size of the smallest FCSR which produces S .


Fibonacci/Galois FCSRs

[Klapper Goresky 02]

Fibonacci setup.

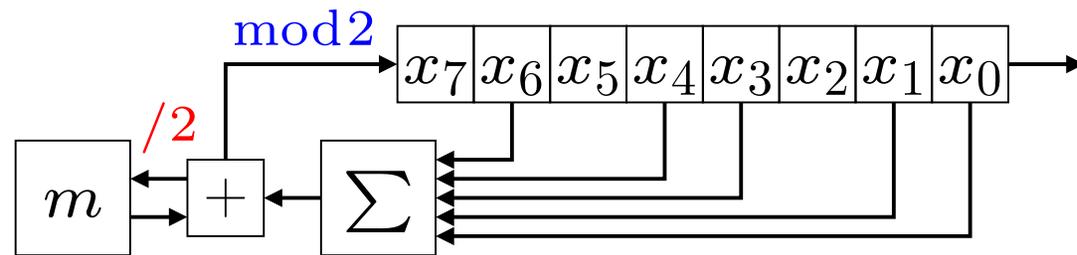


Galois setup.

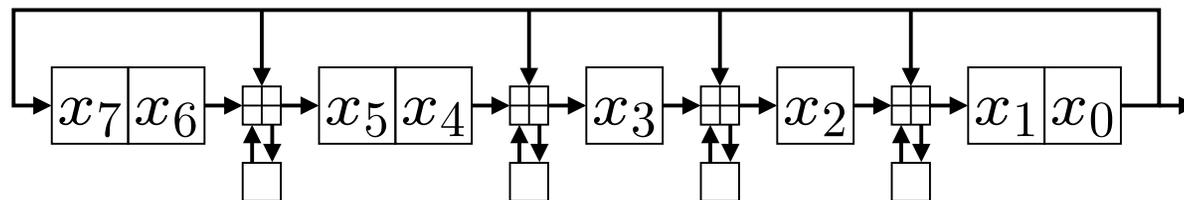

Part 2

LFSRs

Synthesis of Sub-sequences (1)

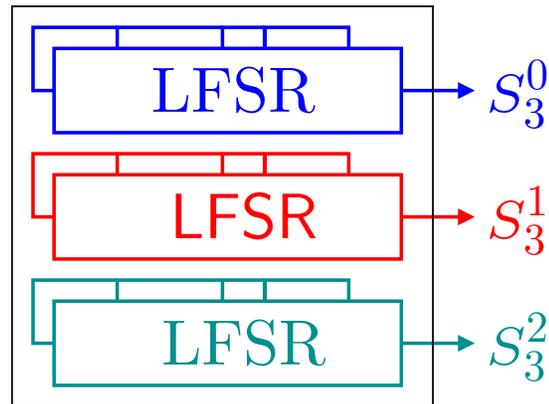

- ▶ Use Berlekamp-Massey algorithm to find the smallest LFSR for each subsequence.
- ▶ **All** sub-sequences are generated using d LFSRs defined by $Q^*(x)$ but initialized with different values.

Synthesis of Sub-sequences (2)

Theorem [Zierler 59]: Let S be produced by an LFSR whose characteristic polynomial $Q(x)$ is irreducible in \mathbb{F}_2 of degree m . Let α be a root of $Q(x)$ and let T be the period of S . For $0 \leq i < d$, S_d^i can be generated by an LFSR with the following properties:

- The minimum polynomial of α^d in \mathbb{F}_{2^m} is the characteristic polynomial $Q^*(x)$ of the new LFSR with:
- Period $T^* = \frac{T}{\gcd(d, T)}$.
- Degree m^* is the multiplicative order of 2 in \mathbb{Z}_{T^*} .

Multiple steps LFSR

[Lempel Eastman 71]

- ▶ Clock d times the register in one cycle.
- ▶ Equivalent to partition the register into d sub-registers

$$x_i x_{i+d} \cdots x_{i+kd}$$

such that $0 \leq i < d$ and $i + kd < m$.


- ▶ Duplication of the feedback:
The sub-registers are linearly interconnected.

Fibonacci LFSR


$$\begin{aligned} \text{next}^1(x_0) &= x_3 \\ \text{next}^1(x_i) &= x_{i-1} \text{ if } i \neq 0 \\ (x_3)_{t+1} &= (x_3)_t \oplus (x_0)_t \\ (x_i)_{t+1} &= (x_{i-1})_t \text{ if } i \neq 3 \end{aligned}$$

$$\begin{aligned} \text{next}^2(x_0) &= x_2 \\ \text{next}^2(x_1) &= x_3 \\ \text{next}^2(x_i) &= x_{i-2} \text{ if } i > 1 \\ (x_i)_{t+2} &= (x_{i-2})_t \text{ if } i < 2 \\ (x_2)_{t+2} &= (x_3)_t \oplus (x_0)_t \\ (x_3)_{t+2} &= \underbrace{(x_3)_t \oplus (x_0)_t}_{(x_3)_{t+1}} \oplus (x_1)_t \end{aligned}$$

1-decimation

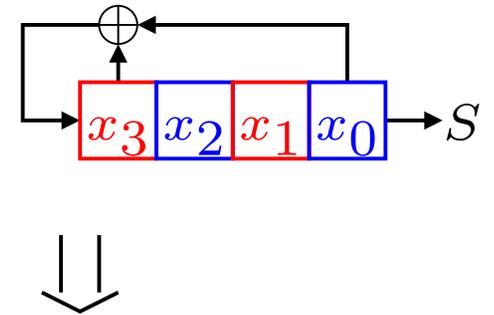

2-decimation

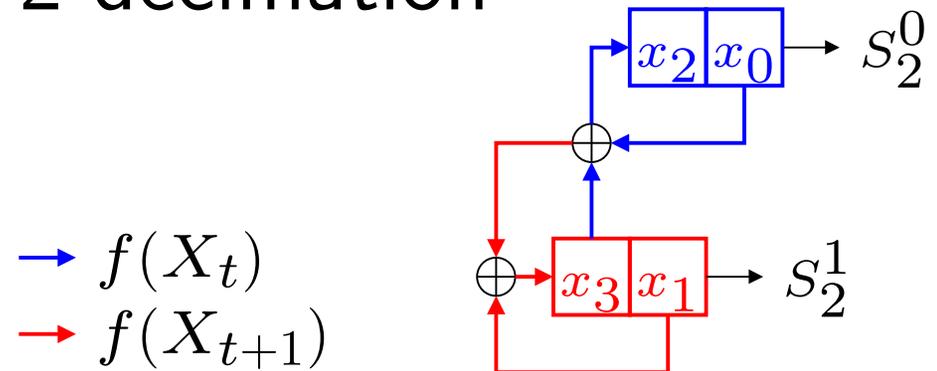


Comparison

Method	Memory cells	Logic Gates
LFSR synthesis	$d \times m^*$	$d \times wt(Q^*)$
Multiple steps LFSR	m	$d \times wt(Q)$

Part 3

FCSRs

Synthesis of Sub-sequences (1)

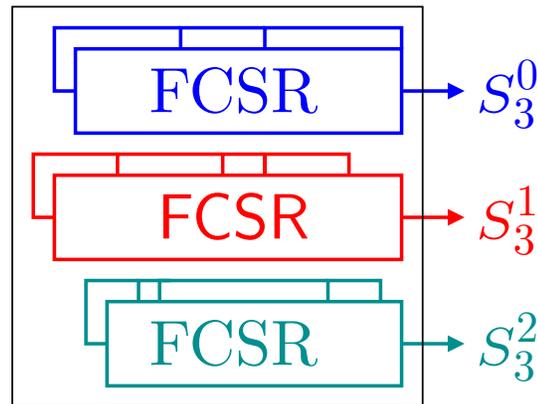

- ▶ We use an algorithm based on Euclid's algorithm [Arnault Berger Necer 04] to find the smallest FCSR for each sub-sequence.
- ▶ The sub-sequences do **not** have the same q .

Synthesis of Sub-sequences (2)

▶ A given S_d^i has period T^* and minimal connection integer q^* .

▶ **Period:** (True for all periodic sequences)

- $T^* \mid \frac{T}{\gcd(T, d)}$,
- If $\gcd(T, d) = 1$ then $T^* = T$.

▶ If $\gcd(T, d) > 1$: T^* might depend on i !

E.g. for $S = -1/19$ and $d = 3$: $T/\gcd(T, d) = 6$.

- S_3^0 : The period $T^* = 2$.
- S_3^1 : The period $T^* = 6$.

Synthesis of Sub-sequences (3)

► **2-adic complexity [Goresky Klapper 97]:**

- General case: $q^* | 2^{T^*} - 1$.
- $\gcd(T, d) = 1$: $q^* | 2^{T/2} + 1$.

► **Conjecture [Goresky Klapper 97]:** Let S be an ℓ -sequence with connection integer $q = p^e$ and period T . Suppose p is prime and $q \notin \{5, 9, 11, 13\}$. For any d_1, d_2 relatively prime to T and incongruent modulo T and any i, j :

$$S_{d_1}^i \text{ and } S_{d_2}^j \text{ are cyclically distinct.}$$

► **Based on Conjecture:** Let q and p be prime and $T = q - 1 = 2p$:

$$\text{If } 1 \leq d < T \text{ and } d \neq p \text{ then } q^* > q.$$

Multiple steps FCSR

- ▶ Clock d times the register in one cycle.
- ▶ Equivalent to partition the register into d sub-registers

$$x_i x_{i+d} \cdots x_{i+kd}$$

such that $0 \leq i < d$ and $i + kd < m$.

- ▶ Interconnection of the sub-registers.
- ▶ Propagation of the carry computation.

Fibonacci FCSR (1)

- ▶ Let the **feedback function** be defined by



$$g(X_t, c_t) = \sum_{j=0}^{m-1} (x_j)_t a_j + c_t$$

- ▶ We can use the following equations:

$$(x_i)_{t+d} = \begin{cases} g(X_{t+d-m+i}, c_{t+d-m+i}) \bmod 2 & \text{if } m-d \leq i < m \\ (x_{i+d})_t & \text{if } i < m-d \end{cases}$$


$$c_{t+d} = g(X_{t+d-m+i}, c_{t+d-m+i}) / 2$$

Fibonacci FCSR (2)

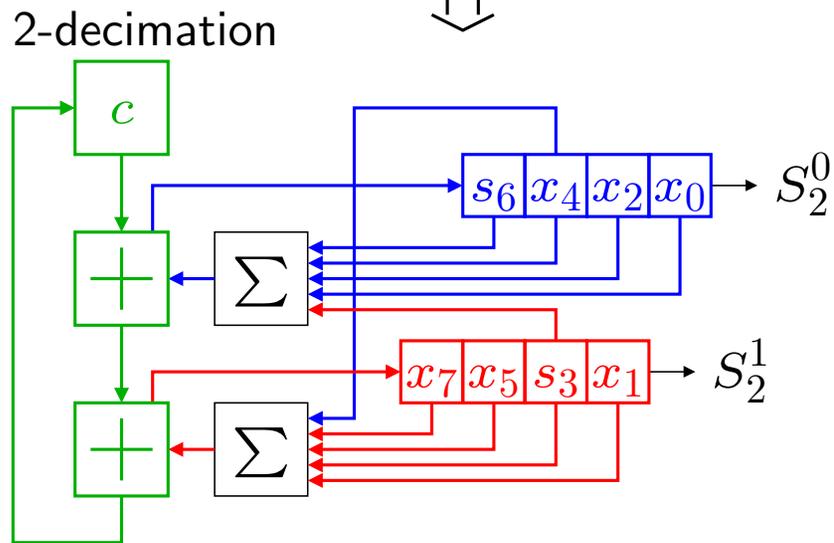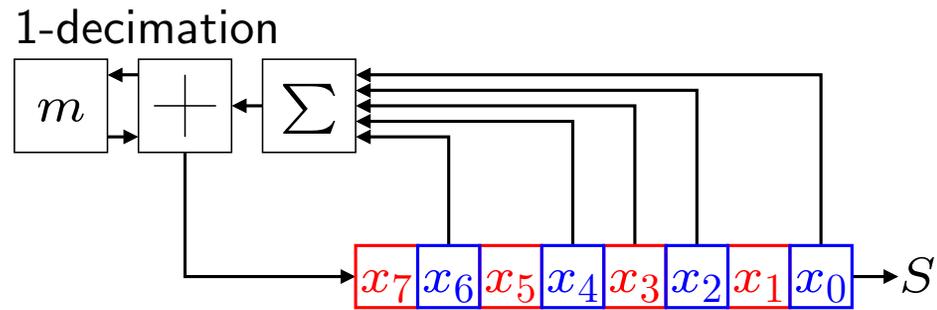

Galois FCSR (1)

- ▶ Example $q = -19$:

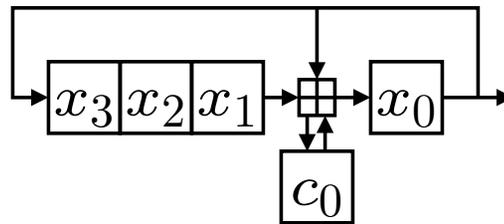

- ▶ Description at the bit-level:

$$\begin{cases} (x_0)_{t+1} = (x_0)_t \oplus (x_1)_t \oplus (c_0)_t \\ (c_0)_{t+1} = [(x_0)_t \oplus (x_1)_t] [(x_0)_t \oplus (c_0)_t] \oplus (x_0)_t \end{cases}$$


Galois FCSR (2)

► $d = 2$, description for the automaton at $t + 1$ and $t + 2$

$$t + 1 \quad \begin{cases} (x_0)_{t+1} = (x_0)_t \oplus (x_1)_t \oplus (c_0)_t \\ (c_0)_{t+1} = [(x_0)_t \oplus (x_1)_t] [(x_0)_t \oplus (c_0)_t] \oplus (x_0)_t \end{cases}$$


$$t + 2 \quad \begin{cases} (x_0)_{t+2} = (x_0)_{t+1} \oplus (x_2)_t \oplus (c_0)_{t+1} \\ (c_0)_{t+2} = [(x_0)_{t+1} \oplus (x_2)_t] [(x_0)_{t+1} \oplus (c_0)_{t+1}] \oplus (x_0)_{t+1} \end{cases}$$

2-bit ripple carry adder

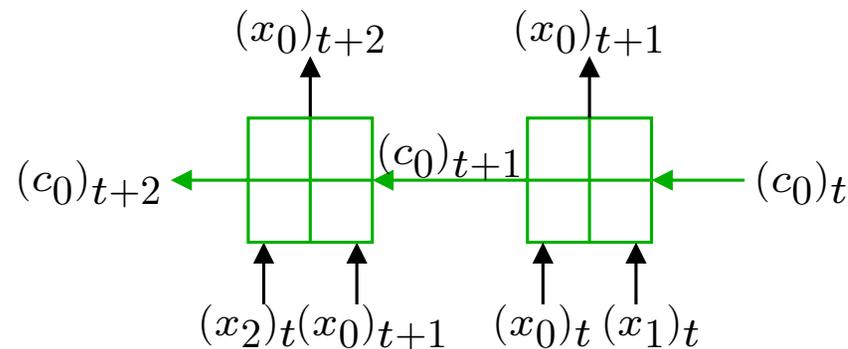


Galois FCSR (3)

1-decimation

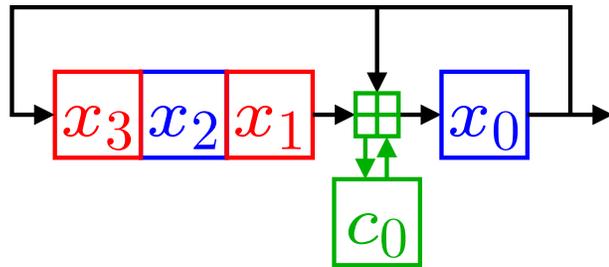

2-decimation

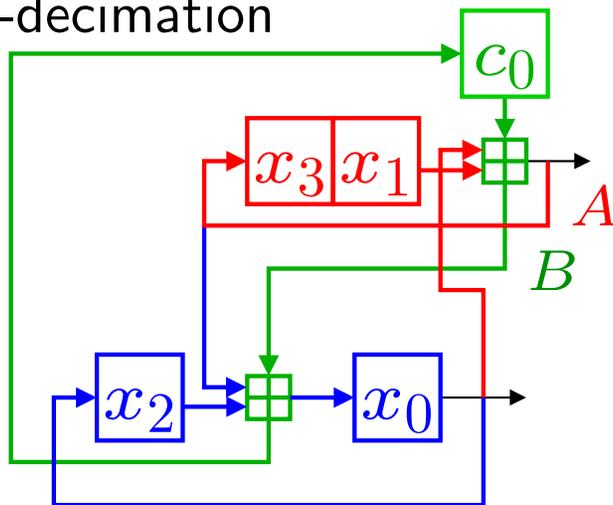

$$A = \boxplus [(x_0)_t, (x_1)_t, (c_0)_t] \bmod 2$$

$$B = \boxplus [(x_0)_t, (x_1)_t, (c_0)_t] \div 2$$

$$(x_0)_{t+2} = \boxplus [A, B, (x_2)_t] \bmod 2$$

$$(c_0)_{t+2} = \boxplus [A, B, (x_2)_t] \div 2$$

$$(x_1)_{t+2} = (x_3)_t$$

$$(x_2)_{t+2} = (x_0)_t$$

$$(x_3)_{t+2} = A$$

Comparison

► Synthesis of Sub-sequences:

- **Period:** If $\gcd(T, d) > 1$ it might depend on i .
- **2-adic complexity:** q^* can be much bigger than q .

► Multiple steps FCSR:

- **Same memory size.**
- Propagation of carry by **well-known arithmetic circuits.**

Part 4

Conclusion

Conclusion

- ▶ The decimation of an ℓ -sequence can be used to increase the throughput or to reduce the power consumption.
- ▶ A separated FCSR for each sub-sequence is not satisfying.

However, the multiple steps FCSR works fine.

- ▶ Sub-expressions simplification:
 - classical for LFSR.
 - new problem for FCSR.